



# 555 Timer Basics

Raspberry Pi

Arduino

DIY Electronics


Programming

Videos

Resources

## ASTABLE MODE

Posted by Scott Campbell | DIY Electronics | 38 🗨️

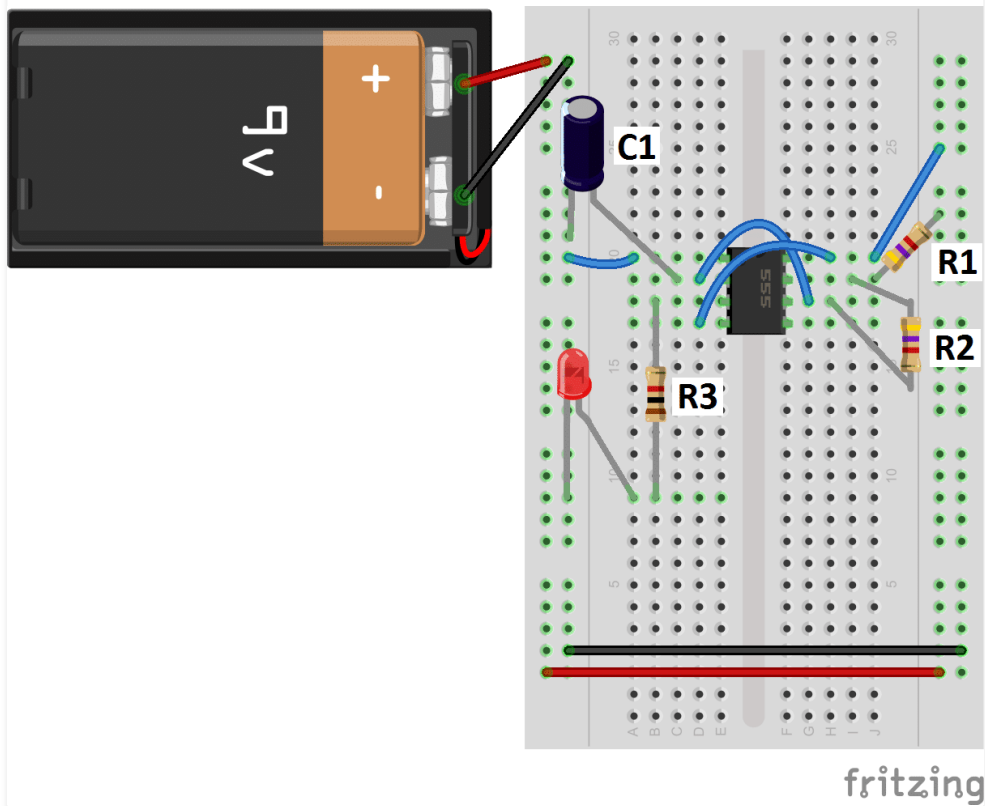


### SUBSCRIBE

Get new  
tutorials sent  
to your inbox!

EMAIL ADD

SUBSCRIBE

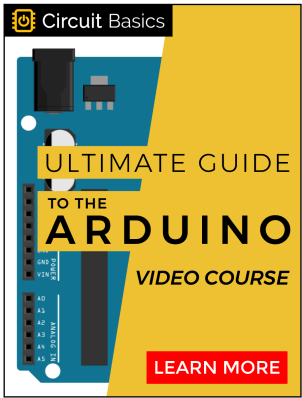

This is part 3 of a series of articles on the 555 timer. Part 1 goes into more detail about the pins and how the chip functions, so you might

want to start there if you haven't read it already: [555 Timer Basics – Monostable Mode](#).



PCBWay PCB Fabrication & Assembly

**ONLY \$5 for 10 PCBs**

- ✓ 24-hour Build Time
- ✓ Quality Guaranteed
- ✓ Most Soldermask Colors:

Order now

## ASTABLE MODE OF THE 555 TIMER

The astable mode is what most people think of when it comes to the [555 timer](#). Many times when you see a project with flashing LEDs, it's a 555 timer at work. But it has a lot of other interesting applications too. For example, it can also generate frequencies to produce sound when the output is connected to a speaker. It can even be used as a simple analog to digital converter (ADC).

BONUS: I made a quick start guide for this tutorial that you can [download](#) and go back to later if you can't set this up right now. It includes all of the wiring diagrams and instructions you need to get started.

In astable mode, the 555 timer acts as an oscillator that generates a square wave. The frequency of the wave can be adjusted by changing the values of two resistors and a capacitor connected to the chip. The formulas below will tell you the length of the output's on and off cycles with different resistors and capacitors:



PCBWay

Professional  
**3D Printing**

**Start from ONLY \$5**

Produces smooth, durable and accurate parts  
50+ Materials Available

Fast & Cheap  
**CNC Machining**

**Start from ONLY \$50**

Machined prototypes in as fast as 1 day  
High-precision tolerances  $\pm 0.005'' - 0.01''$



INSTANT ONLINE TURN-KEY  
QUOTE AND ORDER IN MINUTES

BITTELE  
Turn-Key PCB Assembly

ORDER NOW!

$$t_{on} = 0.69 \times C1 \times (R1 + R2)$$

$$t_{off} = 0.69 \times C1 \times R2$$

$t_{on}$  : Length of high output pulse in seconds

$t_{off}$  : Length of low output pulse in seconds


$R1$  : Resistance of  $R1$  in Ohms

$R2$  : Resistance of  $R2$  in Ohms

$C1$  : Capacitance of  $C1$  in Farads

With this equation, you can see that increasing the values of either  $C1$  or  $R2$  will increase both the time the output stays on and the time it stays off. Increasing the value of  $R1$  will only lengthen the time the output stays on.

## HOW ASTABLE MODE WORKS

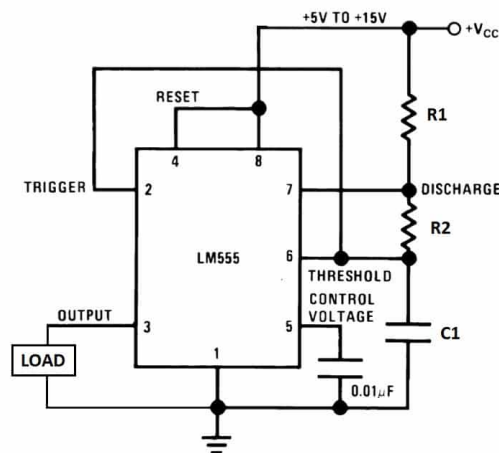

- *Pin 2 – Trigger:* Turns on the output when the voltage supplied to it drops below 1/3 of  $V_{cc}$
- *Pin 6 – Threshold:* Turns off the output when the voltage supplied to it reaches above 2/3  $V_{cc}$ .
- *Pin 7 – Discharge:* When the output voltage is low, it discharges  $C1$  to ground.

In astable mode, the output cycles on and off continuously. In the schematic above, notice that the threshold pin and the trigger pin are

that the threshold pin and the trigger pin are

connected to C1. This makes the voltage the same at the trigger pin, threshold pin, and C1.

At the beginning of an on/off cycle, the voltage is low at C1, the trigger pin, and the threshold pin.


Whenever the trigger pin voltage is low, the output is on, and the discharge pin is off. Since the discharge pin is off, current can flow through resistors R1 and R2, charging capacitor C1.

Once C1 charges to  $2/3 V_{cc}$ , the output is switched off by the threshold pin. When the output goes off, the discharge pin switches on. This allows the charge accumulated on capacitor C1 to drain to ground.

Once the voltage across C1 drops to  $1/3 V_{cc}$ , the trigger pin turns off the discharge pin, so C1 can start charging again.
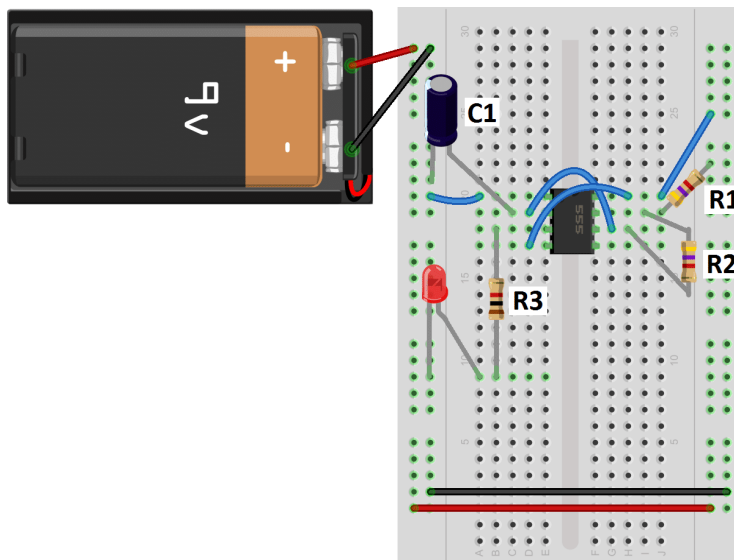
## A BLINKING LED CIRCUIT

To observe the 555 timer in astable mode, let's build a circuit that uses the 555 timer's oscillating output to make an LED flash on and off:




fritzing

- R1: 4.7K Ohm resistor
- R2: 4.7K Ohm resistor
- R3: 1K Ohm resistor
- C1: 100  $\mu$ F capacitor

The values of R1, R2, and C1 affect the speed of the blinking. Larger values will make the LED blink slower, while smaller values will make the LED blink faster. Resistor R3 is just there to limit the current to the LED so it doesn't burn out. If you want to set the blinking to a certain speed, you can use the formula at the beginning of this article to calculate the resistance or capacitance you need.
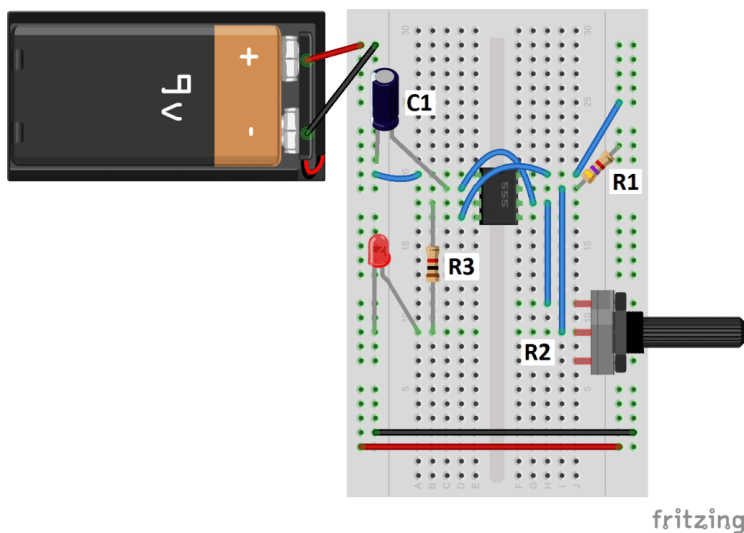
## BLINKING LED CONTROLLED BY A POTENTIOMETER

An easy way to observe the effect of resistance on the blinking speed is to use a **10K Ohm potentiometer** for R2:




- R1: 4.7K Ohm resistor
- R2: 10K Ohm potentiometer
- R3: 1K Ohm resistor

- C1: 100  $\mu$ F capacitor

Adjusting the potentiometer will change the rate of the LED flashing.
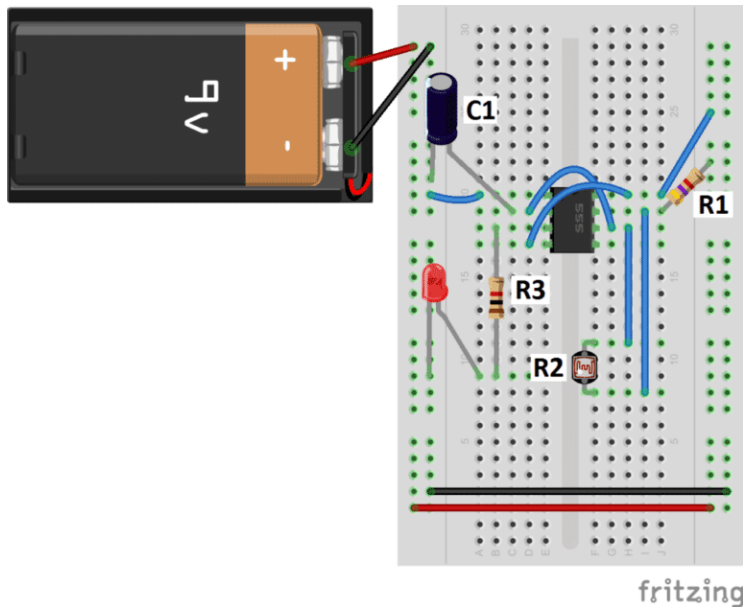
## BLINKING LED CONTROLLED BY A PHOTORESISTOR

Instead of using a potentiometer to control the blinking rate, try connecting a [photoresistor](#):



- R1: 4.7K Ohm resistor
- R2: Photoresistor
- R3: 1K Ohm resistor
- C1: 100  $\mu$ F capacitor

The resistance of a photoresistor decreases as more light shines on it, so the LED will flash more quickly when exposed to more light.

If you want to learn more about the 555 timer, the book [Timer, Op Amp, and Optoelectronic Circuits and Projects Book Vol. 1 By Forrest Mims](#) is a great resource to have on your bench.